
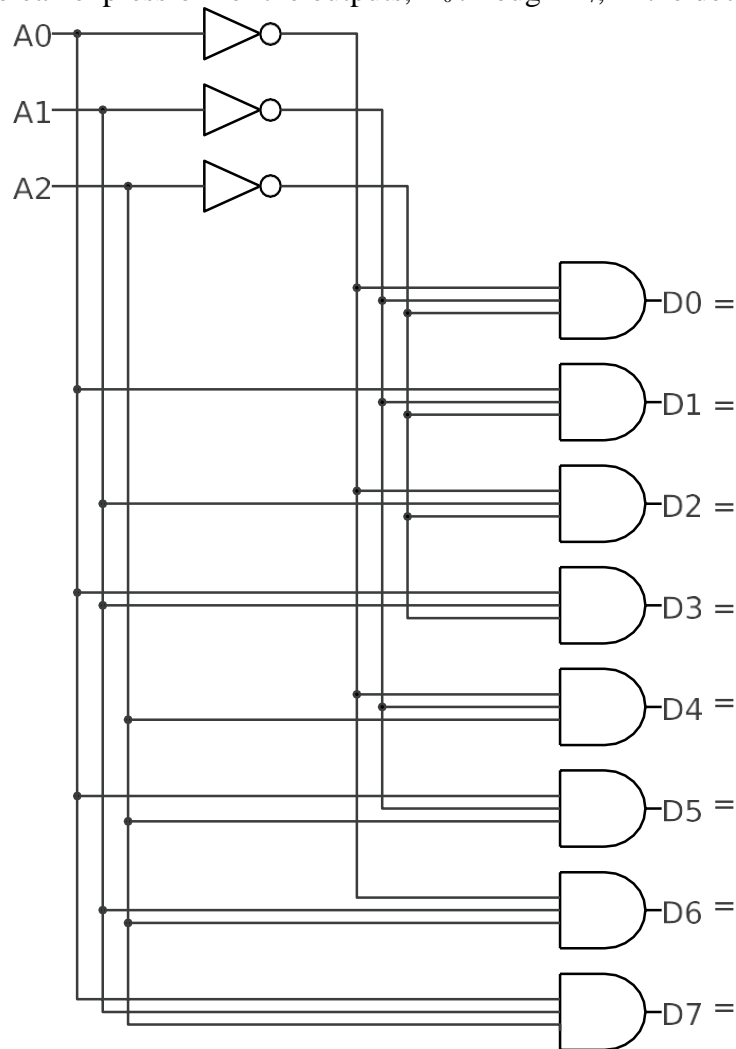


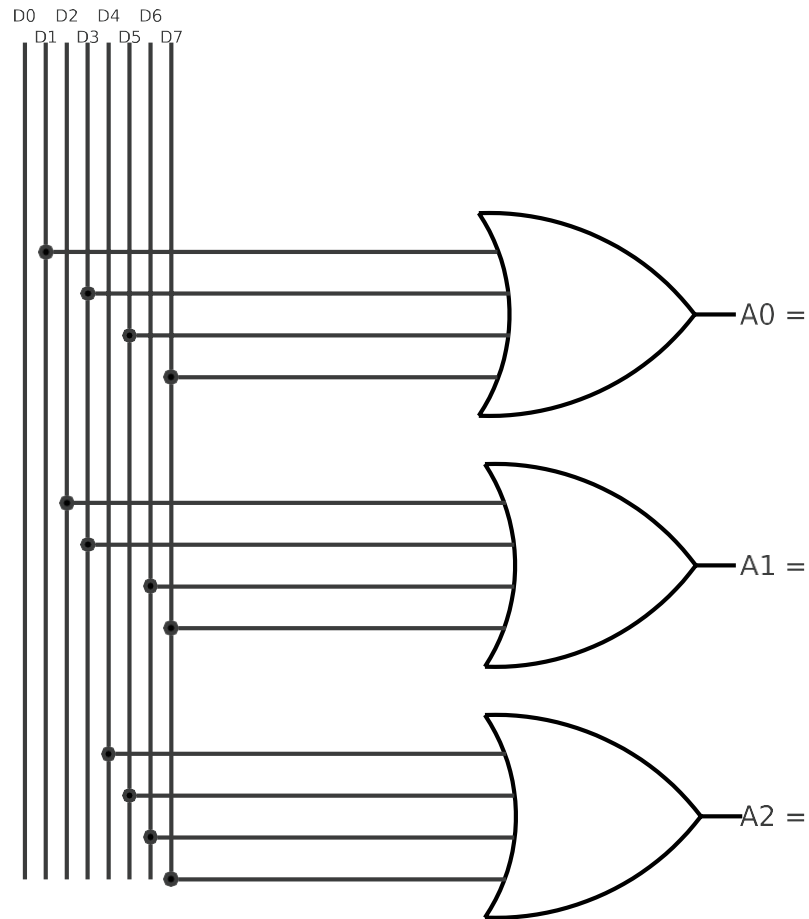1. Provide the Boolean expression for the outputs, D_0 through D_7 , in the decoder below.





Which output would produce a HIGH for an input pattern 110 (A_2, A_1, A_0)?

2. Provide the Boolean expression for the outputs, A_0 through A_2 , in the encoder below.



Which output would be produced if only D_6 was HIGH, and all the other inputs were LOW?

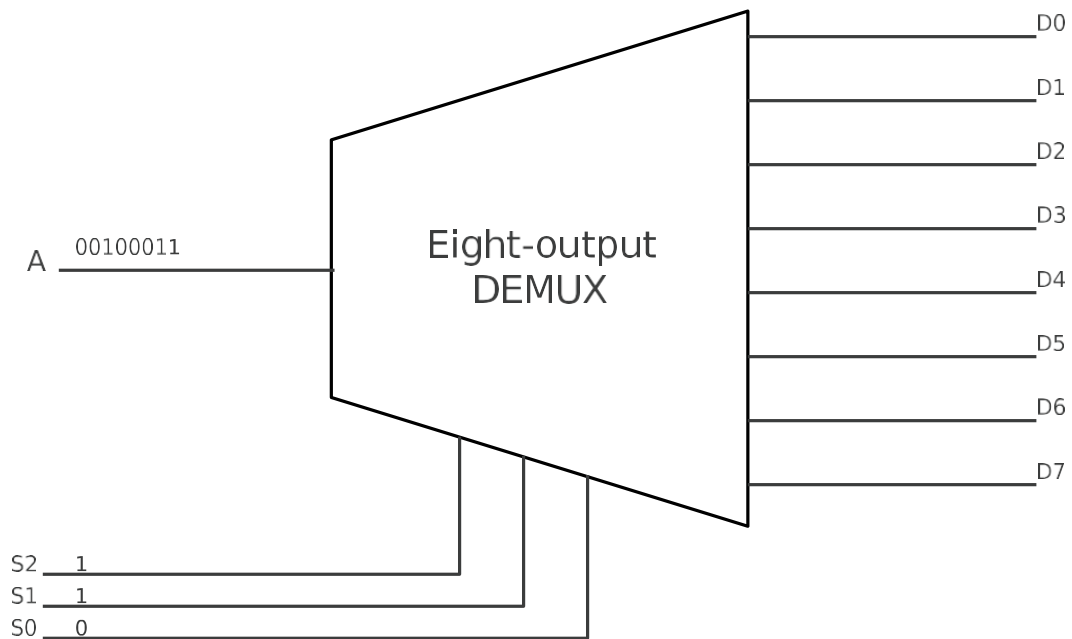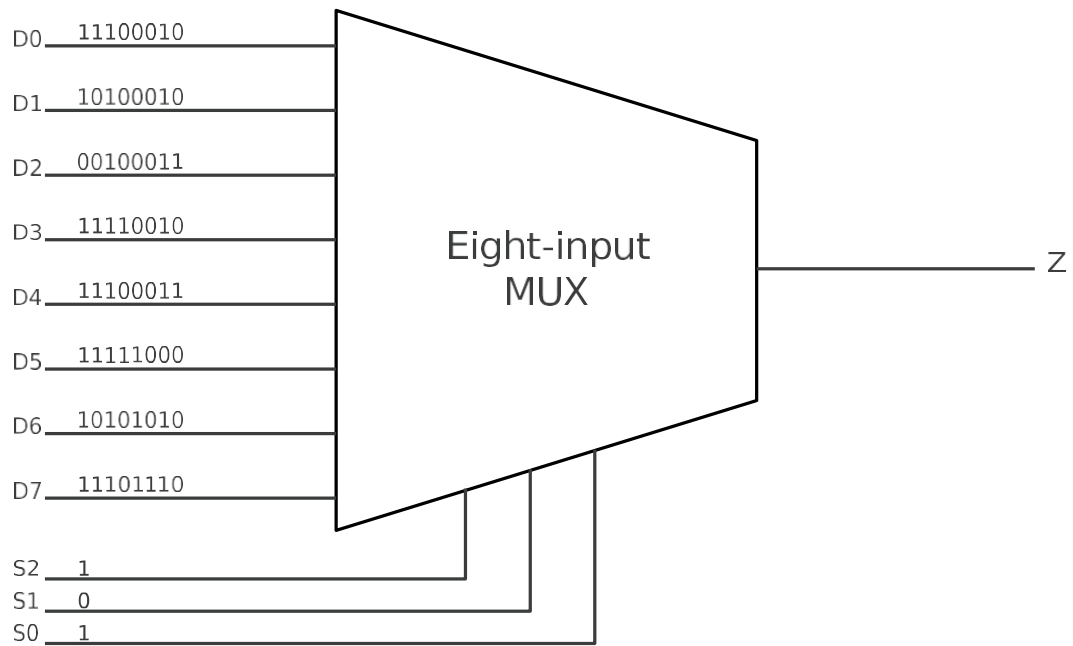3. Show the appropriate outputs for the circuits below:



6. List three special-purpose registers that are important to the operations of the CPU and describe their purpose.

7. A computer simply performs the instruction cycle, over and over. Succinctly describe the instruction cycle, making sure to include appropriate register names and related terms.